

Homework #4

For 01205231 - Electronic Circuits & Systems I, sec 450

Name:

LD:



Due Date: April 21, 2016, 11:59 AM (no late submission)!!

Problem#	Points
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
Total	

Homework # 4 due date April 21, 2016: 11:59 AM

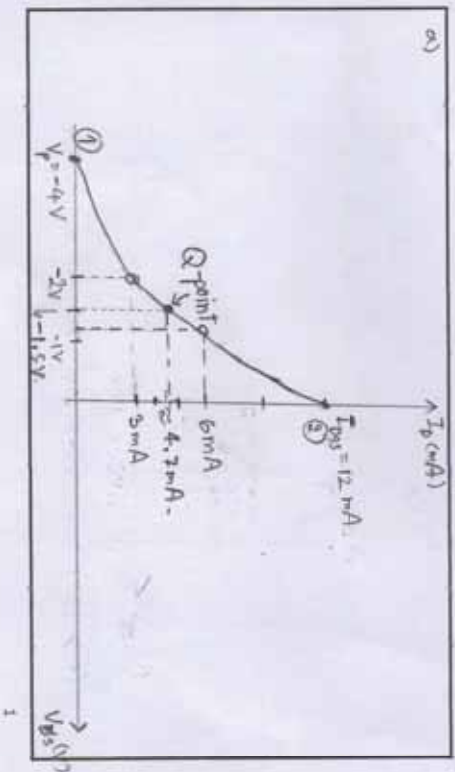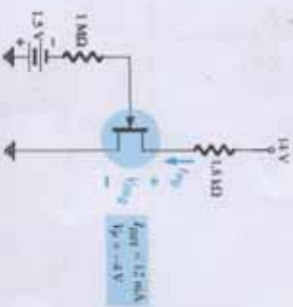1. For the fixed-bias configuration of Figure:

- Sketch the transfer characteristics of the device.
- Superimpose the network equation on the same graph.
- Determine I_{DQ} and V_{DSQ} .
- Using Shockley's equation, solve for I_{DQ} and then find V_{DSQ} . Compare with the solutions of part (c).



(b) Use Shorthand Method to find the point for plotgraph.

① $V_{GS} = V_P = -4V$, $I_D = 0 \text{ mA}$.

② $V_{GS} = 0V$, $I_D = I_{DSS} = 12 \text{ mA}$

③ $V_{GS} = 0.5V_P = -2V$, $I_D = I_{DSS}/4 = 3 \text{ mA}$.

④ $V_{GS} = 0.8V_P = -1.2V$, $I_D = I_{DSS}/2 = 6 \text{ mA}$

(c) From the circuit, there was constant $V_{GS} = -1.5V$

From graph $I_{DQ} = 4.7 \text{ mA}$ ✓

$V_{GS} = V_{DD} - I_{DQ} R_D = 14 - (4.7 \text{ mA})(1.8 \text{ K})$ ✓

$V_{DSQ} = 5.54 \text{ V}$ ✓

(d) Shockley's equation

$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = (12 \text{ mA}) \left(1 - \frac{-1.5}{-4}\right)^2 = 4.68 \text{ mA}$.


$V_{DSQ} = V_{DD} - I_{DQ} R_D = 14 - (4.68 \text{ mA})(1.8 \text{ K})$

$V_{DSQ} = 5.57 \text{ V}$ ✓

2

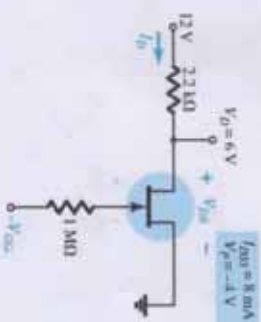2. Given the measured value of r'_D in Figure, determine:

***Please show mathematical equivalent circuit and circle your answers with pen, then write your answer in the provided (pink) box



- a) $I_D = \dots\dots\dots$
b) $r'_{DS} = \dots\dots\dots$
c) $r'_{DS} = \dots\dots\dots$

a) $V_{DD} = V_D + I_D R_D$

$\therefore I_D = \frac{V_{DD} - V_D}{R_D} = \frac{12 - 6}{2.2 \text{ K}} = 2.73 \text{ mA}$ ✓

b) From circuit $V_{GS} = V_D = 6 \text{ V}$ ✓

c) $V_{DS} = -V_{GS}$

Shockley's eq: $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$

$V_{GS} = \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right) V_P$

$= \left(1 - \sqrt{\frac{2.73}{8}}\right) (-4)$



$= -1.66 \text{ V}$

$\therefore V_{DS} = -1.66 \text{ V}$ ✓

3

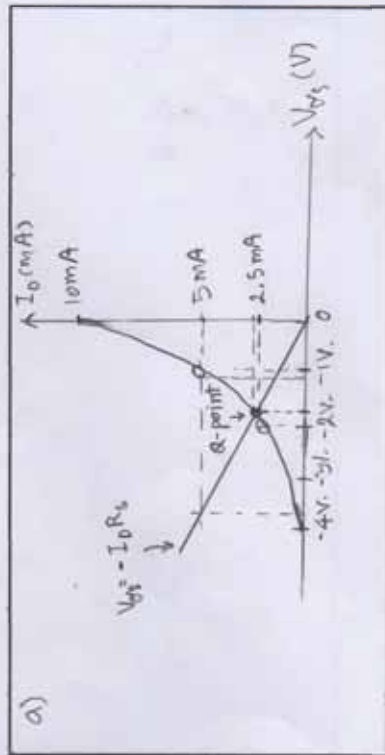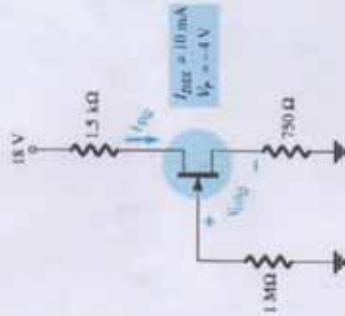3. For the self-bias configuration of Figure:

- Sketch the transfer curve for the device.
- Superimpose the network equation on the same graph.
- Determine I_{DQ} and V_{GSQ} .
- Calculate V_{GS} , V_{DS} , V_{DS} , and V_{GS} .



(b) $V_{GS} = 0V$, $I_{DSS} = 10 \text{ mA}$ ✓
 $V_{GS} = V_P = -4V$, $I_D = 0 \text{ mA}$. ✓
 $V_{GS} = 0.5V_P = -2V$, $I_D = I_{DSS}/4 = 2.5 \text{ mA}$ ✓
 $V_{GS} = 0.5V_P = -1.2V$, $I_D = I_{DSS}/2 = 5 \text{ mA}$ ✓

(c) $V_{GS} = -V_S = -I_D R_S$ — linear equation. ✓
 At $I_D = 5 \text{ mA}$: $V_{GS} = -(5 \text{ mA})(750) = -3.75 \text{ V}$. ✓
 From the graph: $I_{DQ} \approx 2.7 \text{ mA}$ ✓
 $V_{GSQ} = 18 - (2.7 \text{ mA})(1.5 \text{ k} + 0.75 \text{ k})$. ✓
 $V_{GSQ} = 11.925 \text{ V}$. ✓
 $V_{GSQ} = V_P (1 - \sqrt{I_{DQ}/I_{DSS}})$ ✓
 $V_{GSQ} = (-4) (1 - \sqrt{2.7/10}) = -1.92 \text{ V}$. ✓
 (d) $V_D = V_{DD} - I_D R_D = 18 - (2.7 \text{ mA})(1.5 \text{ k}) = 13.95 \text{ V}$. ✓
 $V_G = 0 \text{ V}$ ✓
 $V_S = I_D R_S = (2.7 \text{ mA})(750) = 2.025 \text{ V}$. ✓
 $V_{DS} = V_D - V_S = 13.95 - 2.025 = 11.925 \text{ V}$. ✓

4. Determine I_{DQ} for the network of Figure (Problems 3) using a purely mathematical approach. That is, establish a quadratic equation for I_D and choose the solution compatible with the network characteristics. Compare to the solution obtained in Problem 3.

From Shockley's eq: $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$ — (1)

$$V_{GS} = V_G - V_S = -I_D R_S \quad \text{--- (2)}$$

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{V_P}\right)^2$$

$$I_D = I_{DSS} \left(1 + \frac{2 I_D R_S}{V_P} + \left(\frac{I_D R_S}{V_P}\right)^2\right)$$

$$I_D = I_{DSS} + \left(\frac{2 R_S I_{DSS}}{V_P}\right) I_D + \left(\frac{R_S^2}{V_P^2}\right) I_{DSS} I_D^2$$

$$351.56 I_D^2 - 4.75 I_D + 10^{-2} = 0$$



$$I_D = 0.011, 0.0026$$

$$= \underline{\underline{1.1 \text{ mA}, 2.6 \text{ mA}}}$$

$$\therefore I_{DQ} = 2.6 \text{ mA}$$

$$V_{DSQ} = -(2.6 \text{ mA})(750) = -1.95 \text{ V}$$

5. Find V_S for the network of Figure.

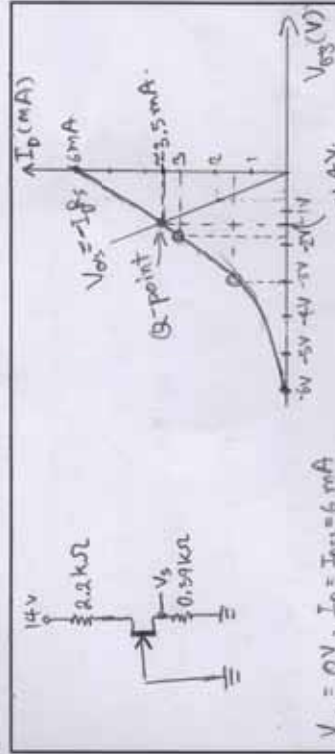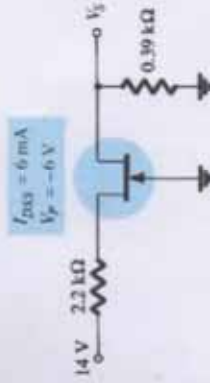

$$V_{GS} = 0 \text{ V}, I_D = I_{DSS} = 6 \text{ mA}$$

$$V_{GS} = V_P = -6 \text{ V}, I_D = 0 \text{ mA}$$

$$V_{GS} = 0.5 V_P = -3 \text{ V}, I_D = 0.25 I_{DSS} = 1.5 \text{ mA}$$

$$V_{GS} = 0.5 V_P = -1.8 \text{ V}, I_D = 0.25 I_{DSS} = 3 \text{ mA}$$


$$V_{GS} = -I_D R_S$$

From graph: $V_{GSQ} \approx -1.4 \text{ V}, I_{DQ} \approx 3.5 \text{ mA}$

$$\therefore V_S \approx -V_{GS} = 1.4 \text{ V}$$

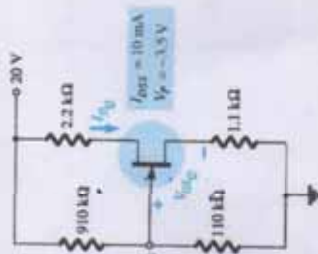6. For the network of Figure, determine:

**Please show methods, equations, circuit and circle your answers with pen; then write your answer in the provided (red) box.



- a) $V_G =$
 b) $I_{DQ} =$
 c) $V_{GS} =$
 d) $V_D =$
 e) $V_S =$
 f) $V_{DS} =$

a) $V_G = \left[\frac{110k\Omega}{(110+910)k\Omega} \right] 20V = 2.16V$ ✓

$V_{GS} = 0.3V_P = -1.05V$, $I_D = 0.5I_{DSS} = 5mA$


$V_{DS} = 0.5V_P = -1.75V$, $I_D = 0.25I_{DSS} = 2.5mA$

$V_{GS} = V_P = -3.5V$, $I_D = 0mA$

$V_{GS} = 0V$, $I_D = I_{DSS} = 10mA$


$V_{DS} = V_G - V_S = 2.16 - I_D R_S$

$V_{GS} = 2.16 - I_D R_S$ ✓

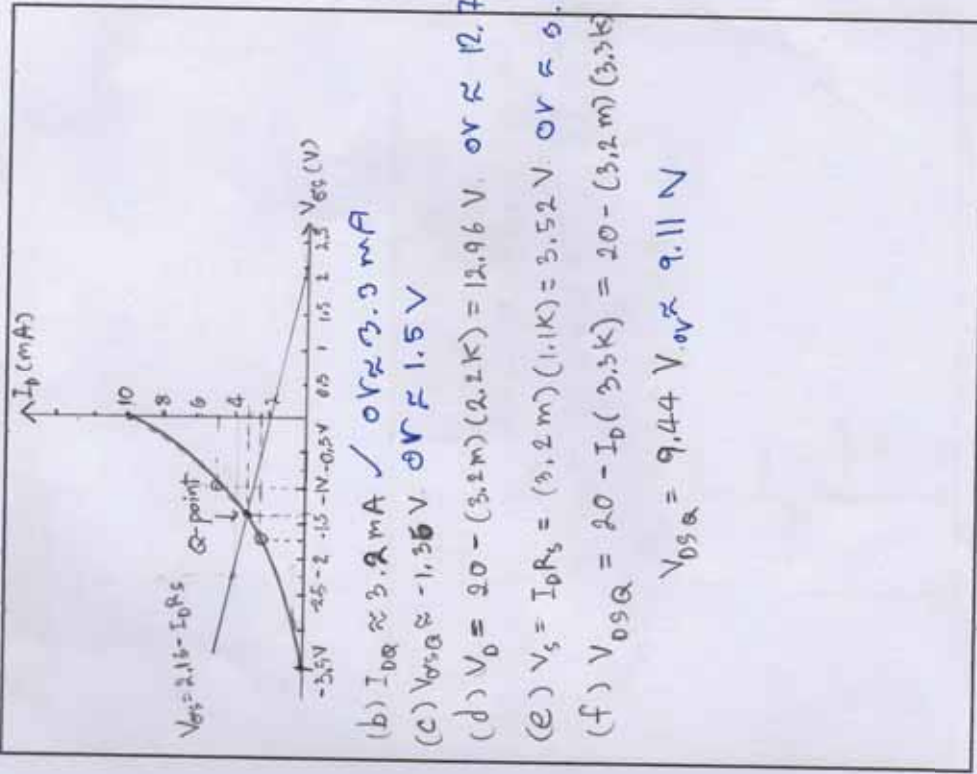

$$V = V - V$$

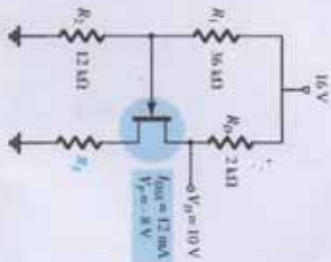7. Determine the value of R_2 for the network of Figure to establish $V_G = 10\text{ V}$.



From Shockley's Equation

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad \text{--- ①}$$

From circuit: $I_D = \frac{16 - V_D}{2k} = \frac{16 - 10}{2k} = 3\text{ mA}$ ✓

$$V_G = \left[\frac{12k\Omega}{(56+12)k\Omega} \right] (16) = 4\text{ V} \quad \checkmark$$

Es, ① we have: $V_{GS} = \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right) V_P = \left(1 - \sqrt{\frac{3}{12}}\right) (-8)$ ✓

$$V_{GS} = -4\text{ V} \quad \checkmark$$


$$\therefore V_S = V_G - V_{GS} = 4 - (-4) = 8\text{ V} \quad \checkmark$$

So $R_S = \frac{V_S}{I_D} = \frac{8}{3\text{ mA}} = 2.67\text{ k}\Omega \rightarrow R_S \text{ can vary.}$ ✓

10

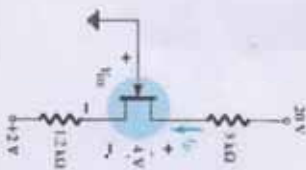8. Given $V_{GS} = 4\text{ V}$ for the network of Figure, determine:

**Please show methods, equivalent circuit and circle your answers with pen, then write your answer in the provided (red) box.



- a) $I_D = \dots\dots\dots$

b) $V_D = \dots\dots\dots$

c) $V_S = \dots\dots\dots$


d) $V_{GS} = \dots\dots\dots$

(a) $I_D = \frac{20 - 4}{(3+12)k} = \frac{16}{15k} \approx 1.07\text{ mA}$ ✓

(b) $V_D = V_{GS} + V_S = 4 + 2 + (0.93\text{ mA})(1.2k) \approx 10\text{ V}$ ✓ $\sqrt{0V - I_D R_D}$

(c) $V_S = V_D - V_{GS} = 10 - 4 = 6\text{ V}$ ✓ $\sqrt{0V - I_D R_S + 2V \approx 5.96V}$

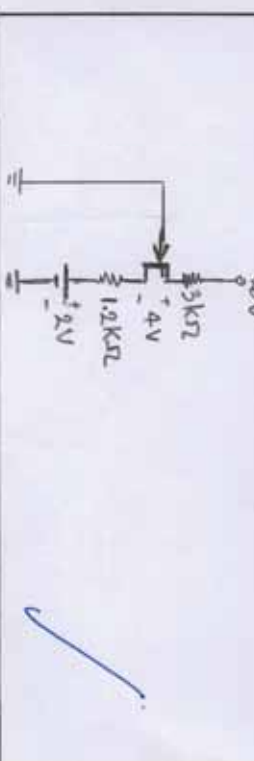(f) $V_{GS} = V_G - V_S = -V_S = -6\text{ V}$ ✓




11

Special Case: $V_{gs} = 0 \text{ V}$

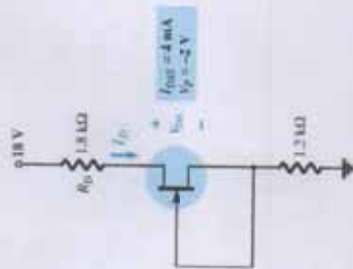9. For the network of Figure

- Find I_{DQ} .
- Determine V_{DS} and V_{GS} .
- Find the power supplied by the source and dissipated by the device.



(a) Because of $V_{GS} = 0 \text{ V}$. So $I_{DQ} = I_{DSS} = 4 \text{ mA}$.

(b) $V_{DQ} = V_{DD} - I_{DQ} R_D = 18 - (4 \text{ mA})(1.8 \text{ k}) = 10.8 \text{ V}$.

$V_{DSQ} = V_{DQ} - V_{GS} = 10.8 - I_{DQ} R_S = 10.8 - (4 \text{ mA})(1.2 \text{ k})$


$\therefore V_{DSQ} = 6 \text{ V}$

(c) $P_{src} = I_D V_{DD} = (4 \text{ mA})(18) = 72 \text{ mW}$

$P_{device} = I_D V_{DS} = (4 \text{ mA})(6) = 24 \text{ mW}$

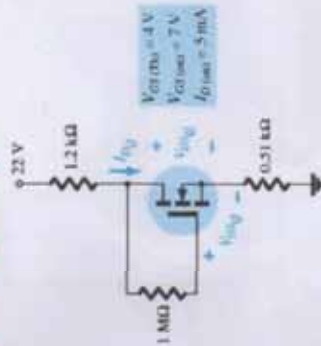10. For the network of Figure, determine:

**Please show methods, equivalent circuit and circle your answers with pen, then write your answer in the provided (red) box.



- a) $I_{DQ} =$
 b) $V_{DSQ} =$
 c) $V_{GSQ} =$
 d) $V_S =$
 e) $V_D =$
 f) $V_{DS} =$

(a) $I_{DQ} = k(V_{GS} - V_T)^2$
 From $k = \frac{I_{D(on)}}{(V_{GS(on)} - V_T)^2} = \frac{5mA}{(7 - 4)^2 V^2} = 0.56 \times 10^{-3} \frac{A}{V^2}$
 $\therefore I_{DQ} = (0.56 \times 10^{-3})(V_{GS} - 4)^2$ — The transfer characteristics eq.
 From circuit: $V_{DS} = V_{DS} + I_D(R_S + R_D)$ — linear eq.
 ① if $V_{DS} = 0$; $I_D = \frac{V_{DS}}{R_S + R_D} = \frac{22}{1.27k} = 12.86mA$
 ② $I_D = 0$; $V_{DS} = V_{DD} = 22V$
 $V_{DS} = V_{DS} - V_{GS} \rightarrow V_{GS} = V_{DS}$; $V_{DS} = 0$


plot graph.

or from graph
 $I_{DQ} \approx 8.28mA$
 $V_{DSQ} \approx 7.9V$

(b) Intersections point of curve and line.
 $(0.56 \times 10^{-3})(V_{GS} - 4)^2 = \frac{V_{DD} - V_{GS}}{R_S + R_D}$
 $(0.56 \times 10^{-3})V_{GS}^2 - (8.95 \times 10^{-3})V_{GS} - (3.9 \times 10^{-3}) = 0$
 $V_{GS} = -0.89, 7.84V$
 $\therefore I_{DQ} = \frac{22 - 7.84}{1.27k} = 8.28mA$
 (c) $V_{DSQ} = V_{GSQ} = 7.84V$
 (d) $V_D = 22 - (8.28m)(1.2k) = 12.064V \Rightarrow V_D = 12.06V$
 (e) $V_S = (8.28)(0.31) = 4.223V$
 (f) $V_{DS} = 12.064 - 4.223 = 7.84V$

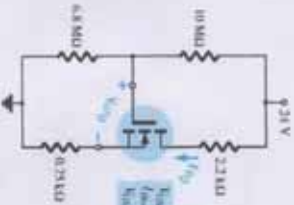11. For the voltage-divider configuration of Figure, determine:

**Please show methods, equivalent circuit and circle your answers with pen, then write your answer in the provided (red) box.



- a) $I_{DQ} = \dots\dots\dots$
 b) $V_{DSQ} = \dots\dots\dots$
 c) $V_S = \dots\dots\dots$
 d) $V_G = \dots\dots\dots$

a) From Eq. $I_D = K(V_{GS} - V_T)^2$

$K = \frac{I_{DQ}}{(V_{GSQ} - V_T)^2} = \frac{5 \text{ mA}}{(6 - 3)^2} = 0.55 \times 10^{-3}$

$V_{GSQ} = V_G - V_S = \frac{(6.8)24}{(16.8)} - I_D(0.75k)$

$V_{GSQ} = 9.71 - 750I_{DQ}$

$V_T = 3V$

$I_{DQ} = (0.55 \times 10^{-3})(6.71 - 750I_{DQ})^2$

$509.375 I_{DQ}^2 - 5.53 I_{DQ} + 0.025 = 0$


$I_{DQ} = 16 \mu A, 5 \text{ mA}$

b) $V_{DSQ} = 9.71 - (750)(5 \times 10^{-3}) = 5.96 \text{ V}$

c) $V_D = 9.71 - (5)(2.2) = 13 \text{ V}$

d) $V_S = (0.75)(5) = 3.75 \text{ V}$

from problem.

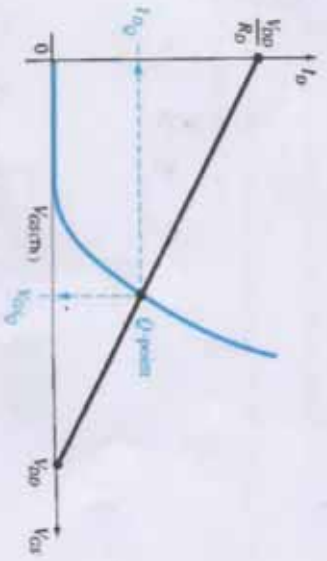

12. Design a network such as appears in Figure using an enhancement-type MOSFET with $V_{DSQ} = 4V$ and $k = 0.5 \times 10^{-3} A/V^2$ to have a Q-point of $I_{DQ} = 6 \text{ mA}$. Use a supply of 16 V and standard values.

From eq: $I_{DQ} = K(V_{GSQ} - V_T)^2$

$6 \times 10^{-3} = (0.5 \times 10^{-3})(V_{GSQ} - 4)^2$

$(0.5 \times 10^{-3})V_{GSQ}^2 - 4 \times 10^{-3}V_{GSQ} + 8 \times 10^{-3} = 0$

$V_{GSQ} = 7.46 \text{ V}, 0.95 \text{ V}$

$V_{GSQ} = V_{DSQ} + I_{DQ}R_D$

$V_{DS} = V_{DS} + I_{DQ}R_D$


From $V_{DS} = V_{DS} - V_{DS}$

$0 = V_{DS} - V_{DS}$

$\therefore V_{DS} = V_{DS}$

$\therefore R_D = \frac{V_{DD} - V_{DSQ}}{I_{DQ}} = \frac{16 - 7.46}{6 \text{ mA}} = 1.42 \text{ k}\Omega$

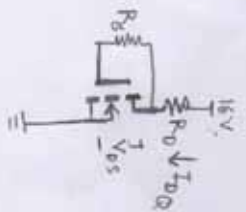R_G should have very high value: such as $1 \text{ M}\Omega$. In order to limit the I_G .



$I_{DQ} = K(V_{GSQ} - V_T)^2$

$\frac{I_{DQ}}{K} = (V_{GSQ} - V_T)^2$

$\sqrt{\frac{I_{DQ}}{K}} = V_{GSQ} - V_T$

$\sqrt{\frac{6 \text{ mA}}{0.5 \text{ mA/V}^2}} = V_{GSQ} - 4$

$\sqrt{12} = V_{GSQ} - 4$

$3.46 = V_{GSQ} - 4$

$V_{GSQ} = 7.46 \text{ V}$

$V_{DSQ} = V_{DSQ} + I_{DQ}R_D$

$4 = 4 + 6R_D$

$0 = 6R_D$

$R_D = 0$

$R_D = 1.42 \text{ k}\Omega$