

Introduction

FET (Field-effect transistor)

- High input impedance
- Low power consumption
- Control an output drain current by a small input voltage (gate voltage)
- Widely use in high-frequency application


BJT = Current control device

FET = Voltage control device

BJT has β (beta)


FET has g_m transconductance factor

JFET

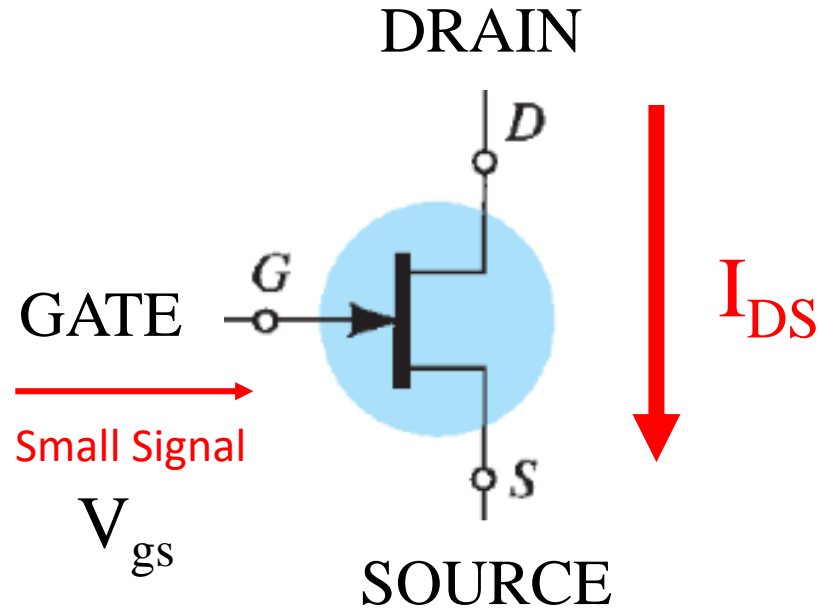



- Input AC voltage to Gate-Source
- The main current I_{DS} is controlled
- No current flow from gate
- Very high input impedance
- Current Gain = ∞

Fixed-Bias Configuration

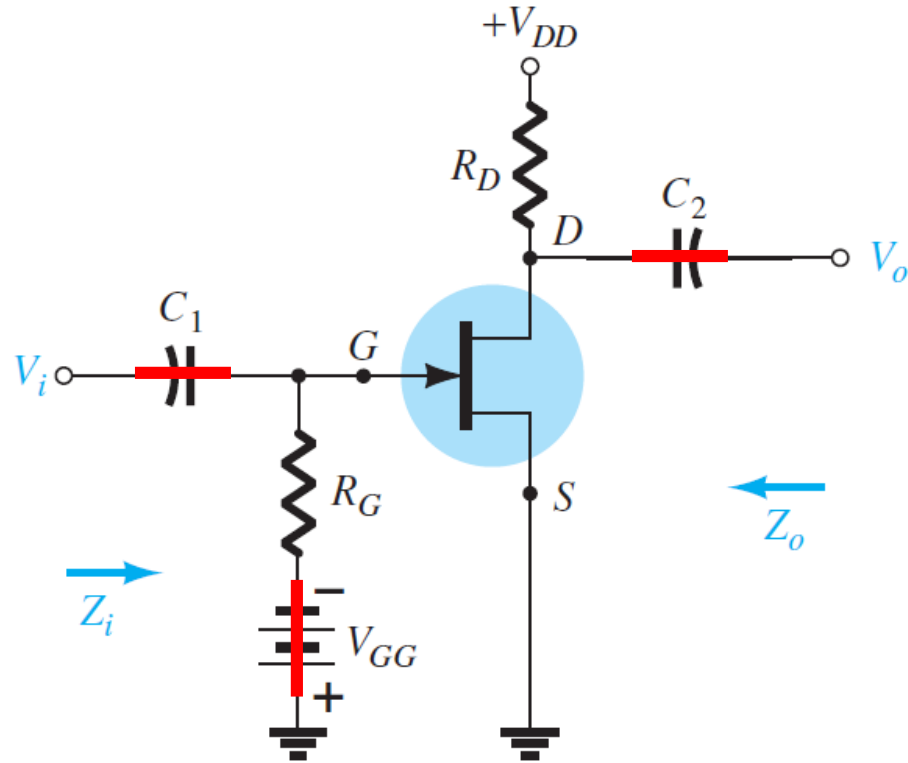


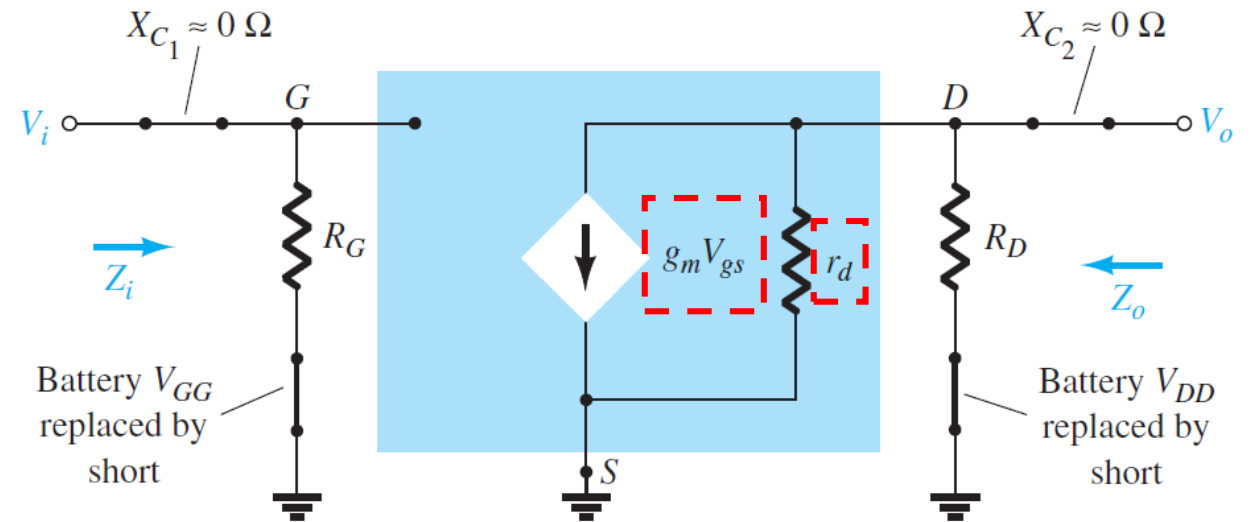- In case of ac analysis, the ac equivalent model is used.
- Small signal analysis is necessary.
- Short source, Short C and redraw



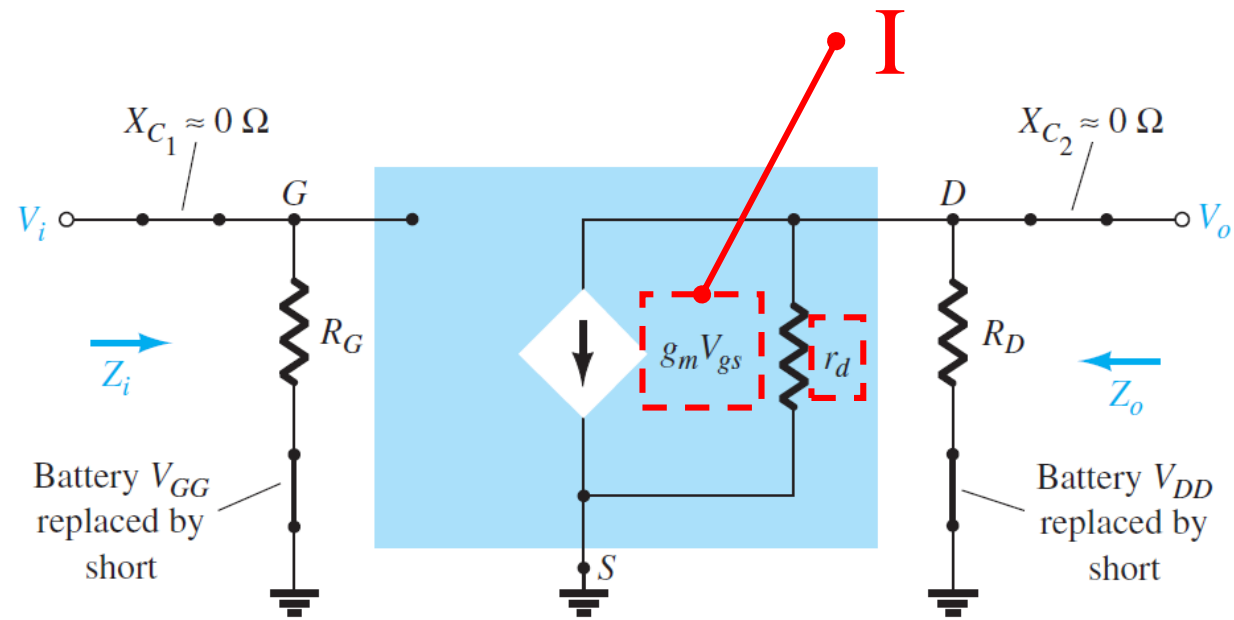

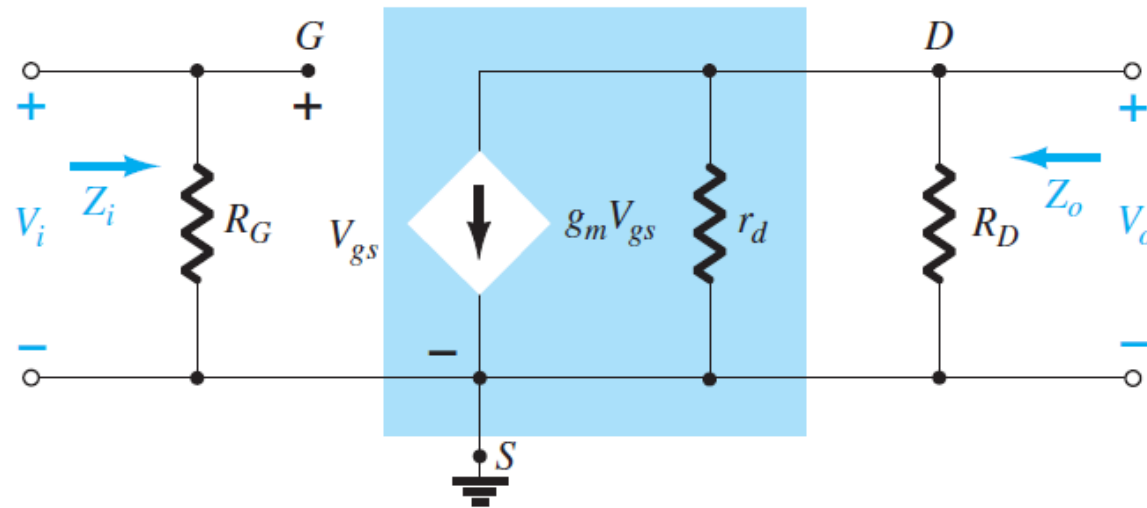
Connect ground,
obtain ac equivalent circuit



$$G = \frac{1}{R}$$

Conductance

Find Parameters

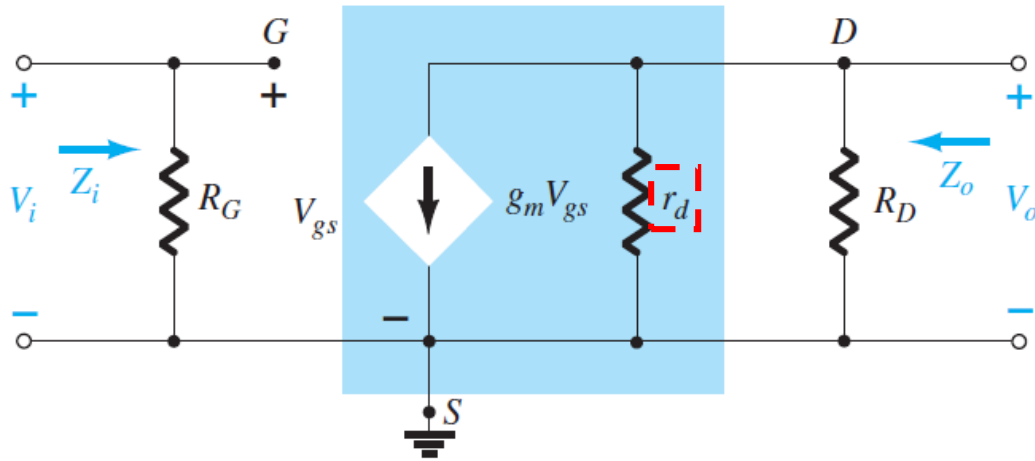

$$Z_i = R_G$$

$$Z_o = R_D \parallel r_d$$

See next slide

$$Z_o \cong R_D$$

$$r_d \geq 10R_D$$

Good switch

r_d High or Low ??

$$A_v = \frac{V_o}{V_i} = -g_m R_D$$

$$r_d \geq 10R_D$$

Find gain A_v

$$V_o = -g_m V_{gs} (r_d \parallel R_D)$$

$$= -g_m V_i (r_d \parallel R_D)$$

Minus sign means
inverse phase i/p and o/p

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

Z_o

- Short input source $V_i = 0$ V


$V_{gs} = 0$ V

$g_m V_{gs} = 0$ mA

means

Current Source = $g_m V_{gs}$ open circuit,
no current flow

Finally we obtain the equivalent circuit

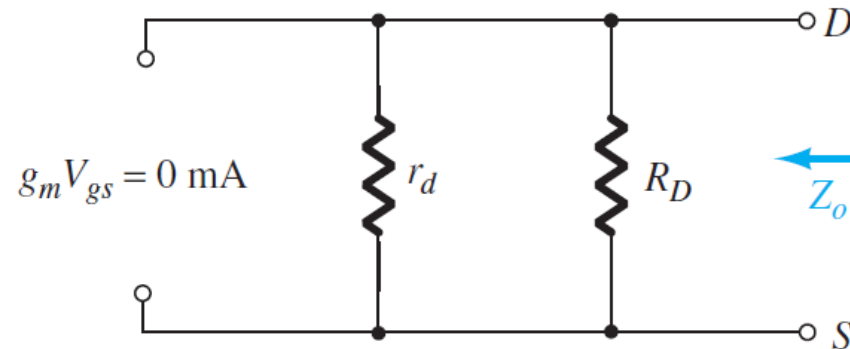

Small Signal Analysis

Shockley's equation (From Ch.6)

Show ac input G to S can
control current level on D to S



control variable

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

constants


transconductance factor g_m

$$\Delta I_D = g_m \Delta V_{GS}$$

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

→ Drain current changing


Current to Voltage ratio

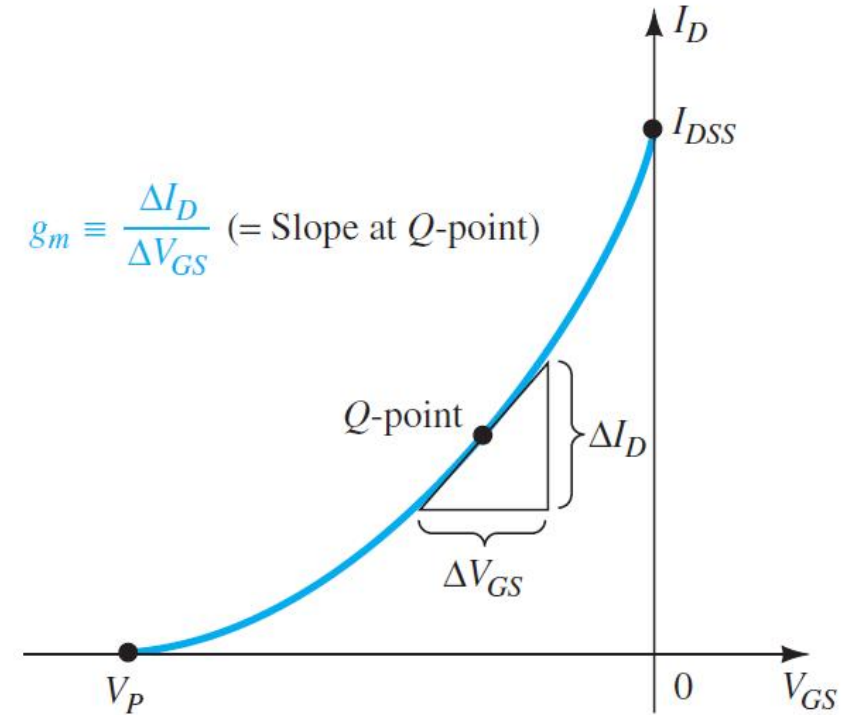

Transfer Characteristic Curve

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$

Mathematical Definition of g_m

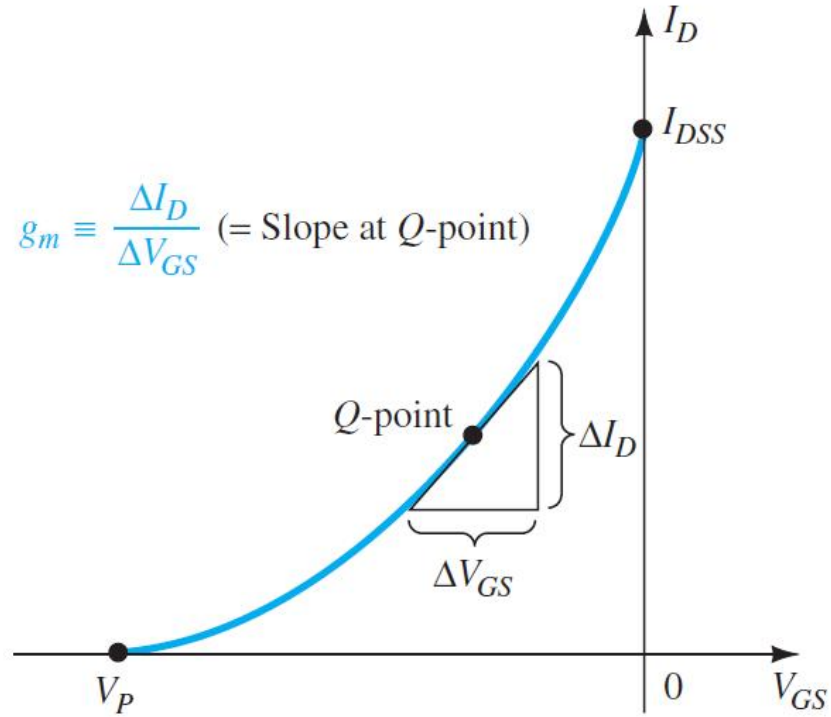

Transfer Characteristic Curve


$$\begin{aligned} g_m &= \left. \frac{dI_D}{dV_{GS}} \right|_{Q\text{-pt.}} = \frac{d}{dV_{GS}} \left[I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \right] \\ &= I_{DSS} \frac{d}{dV_{GS}} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 2I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \frac{d}{dV_{GS}} \left(1 - \frac{V_{GS}}{V_P} \right) \\ &= 2I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \left[\frac{d}{dV_{GS}} (1) - \frac{1}{V_P} \frac{dV_{GS}}{dV_{GS}} \right] = 2I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \left[0 - \frac{1}{V_P} \right] \end{aligned}$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$



$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right]$$


$$Z_i, Z_o, r_d$$

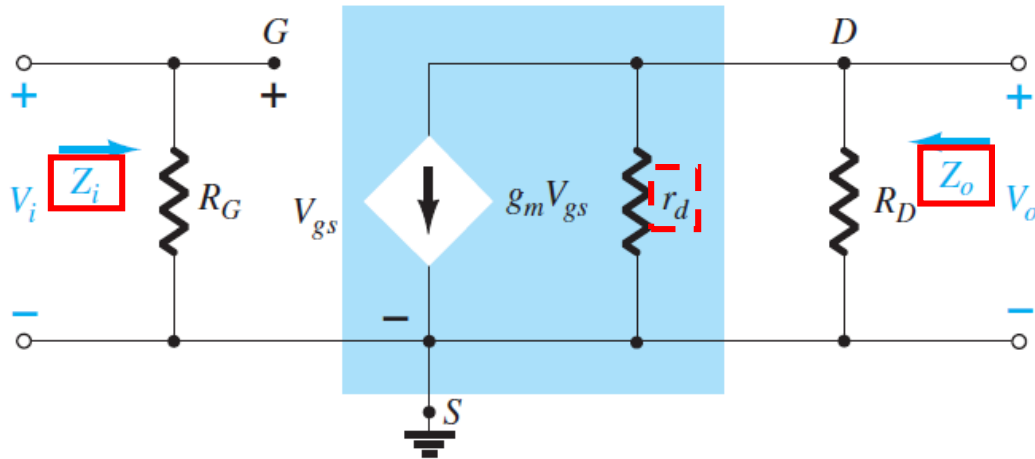

$$Z_i (\text{JFET}) = \infty \Omega$$

$$Z_o (\text{JFET}) = r_d = \frac{1}{g_{os}} = \frac{1}{y_{os}}$$

admittance

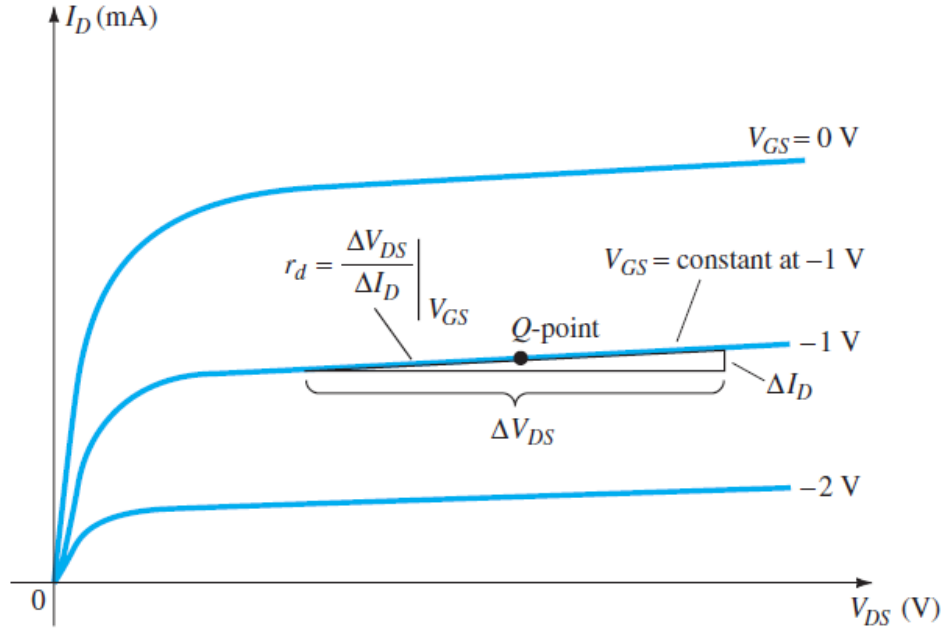


Definition of r_d using JFET drain characteristics

$$r_d = \frac{\text{นอก}}{\text{ดิ่ง}}$$

Large $r_d \rightarrow$ Slope??

Small $r_d \rightarrow$ Slope??


Fixed-Bias Configuration

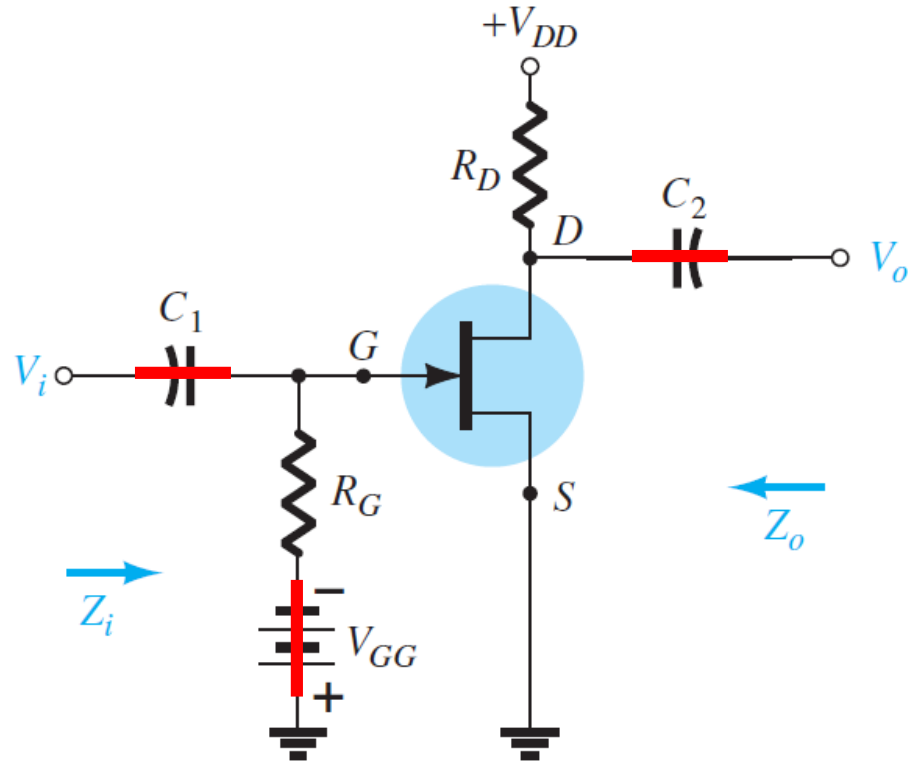


See Example 8.7

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$

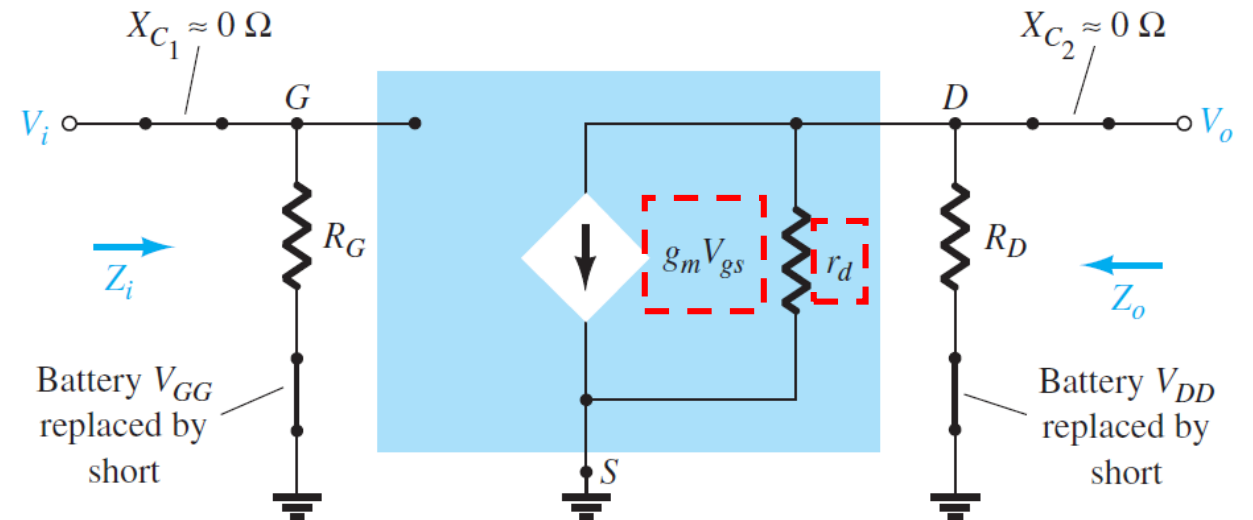
$$Z_o (\text{JFET}) = r_d = \frac{1}{g_{os}} = \frac{1}{y_{os}}$$



Self-Bias Configuration (bypass R_s)

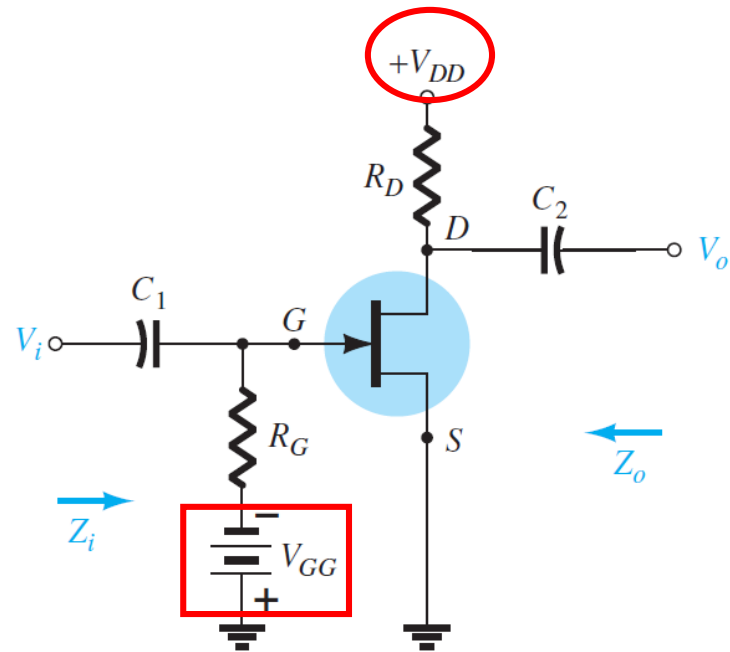



Fixed-Bias Configuration

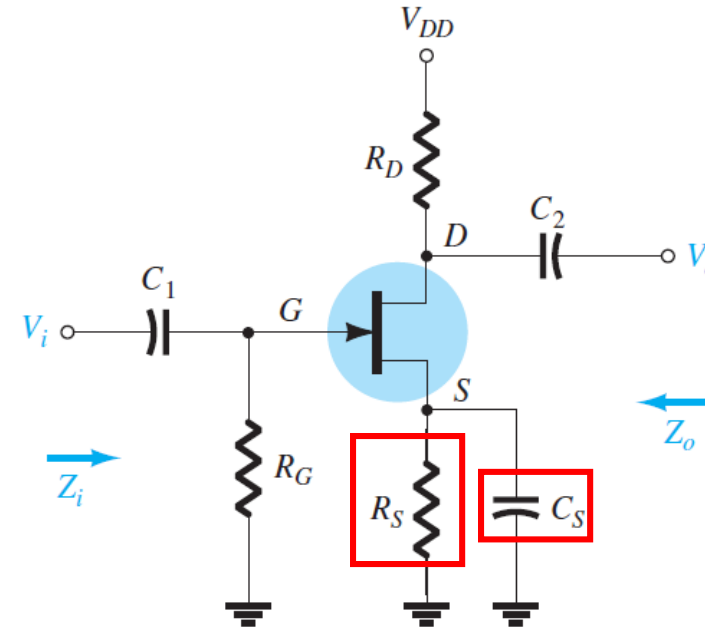

Self-Bias Configuration

Demerit: 2 voltage sources

AC Equivalent Circuit

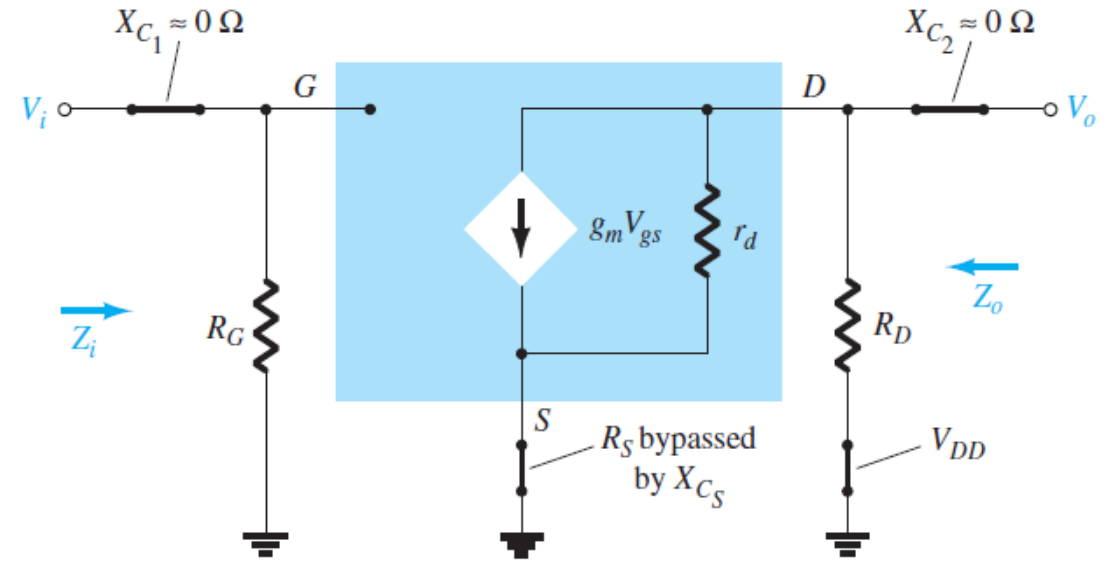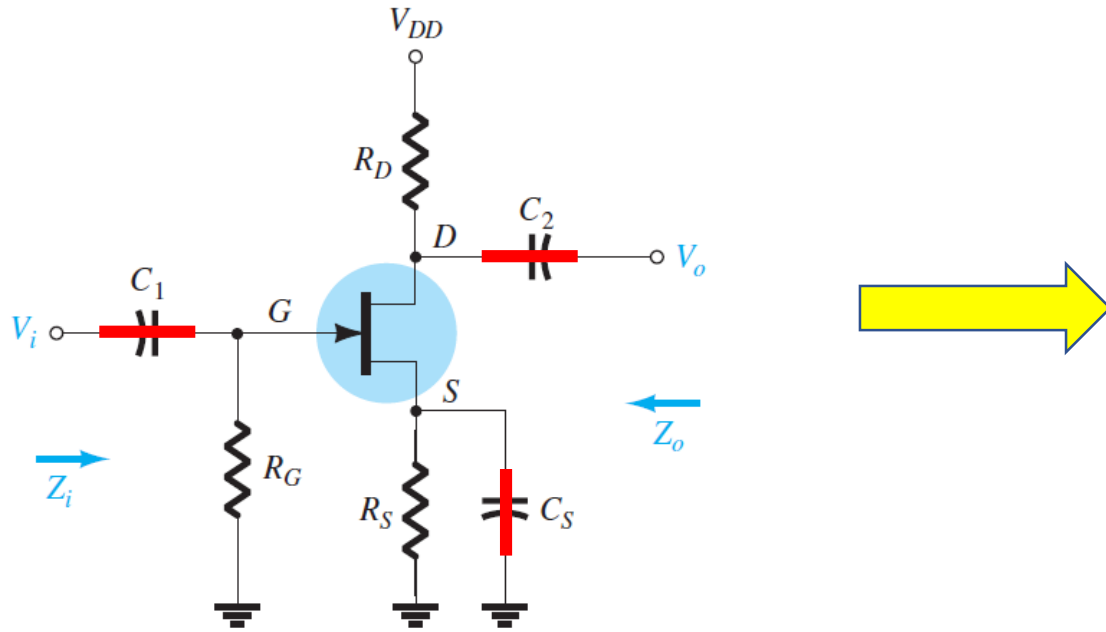


$$Z_i = R_G$$

$$A_v = -g_m(r_d \parallel R_D)$$





$$Z_o = r_d \parallel R_D$$

$$A_v = -g_m R_D$$

$$Z_o \cong R_D$$

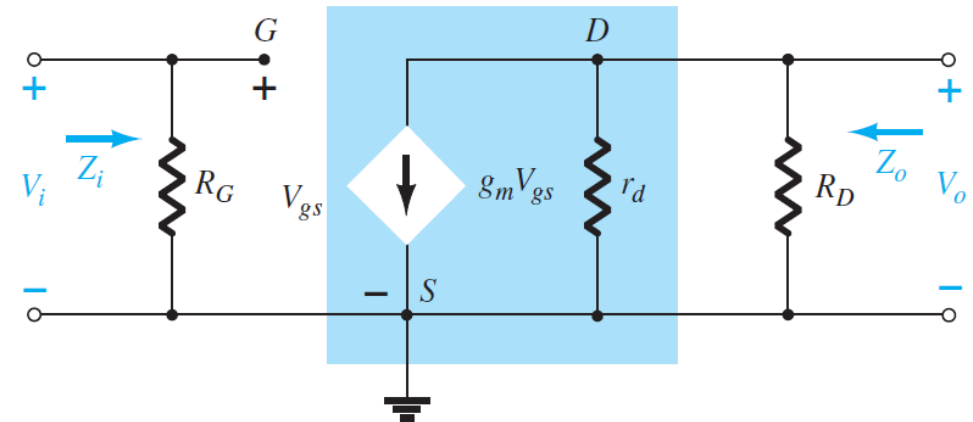

VOLTAGE-DIVIDER CONFIGURATION

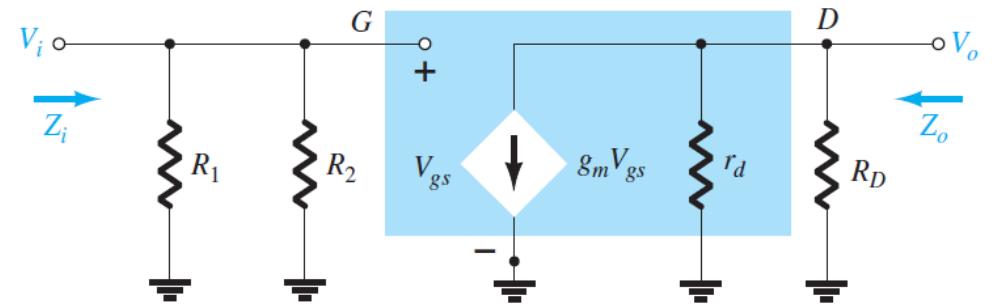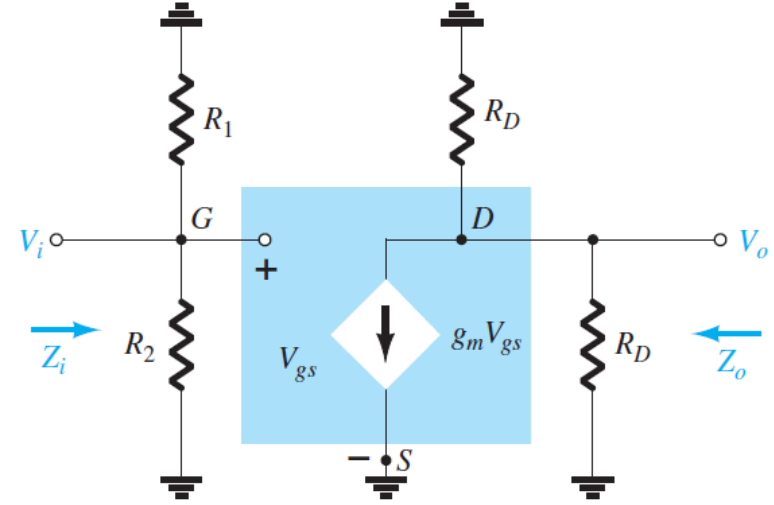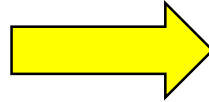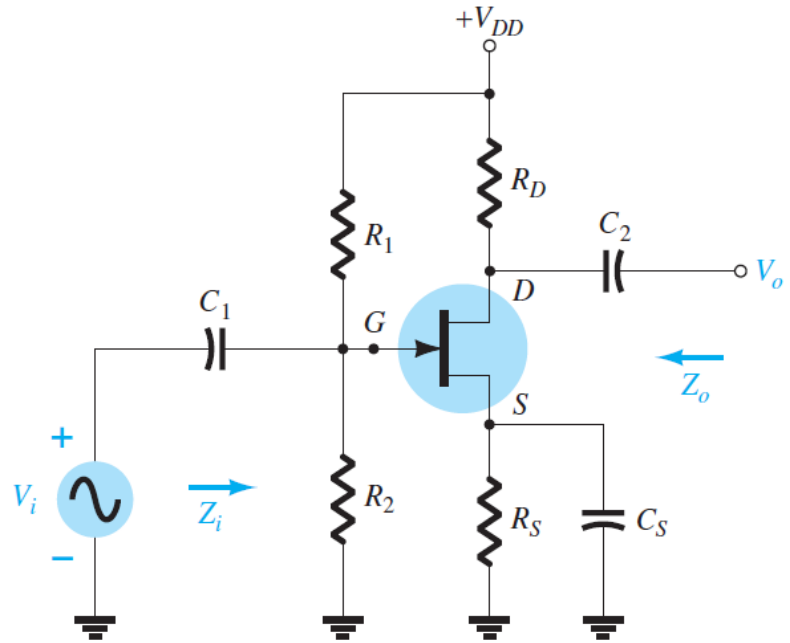

$$Z_i = R_1 \parallel R_2$$


$$Z_o \cong R_D$$

$$r_d \geq 10R_D$$



$$Z_o = r_d \parallel R_D$$


$$A_v = \frac{V_o}{V_i} = -g_m(r_d \parallel R_D)$$

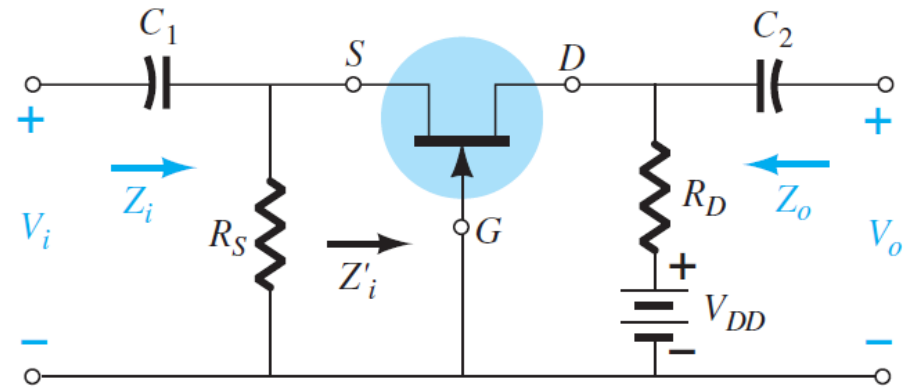COMMON-GATE CONFIGURATION / (COMMON-GROUND)



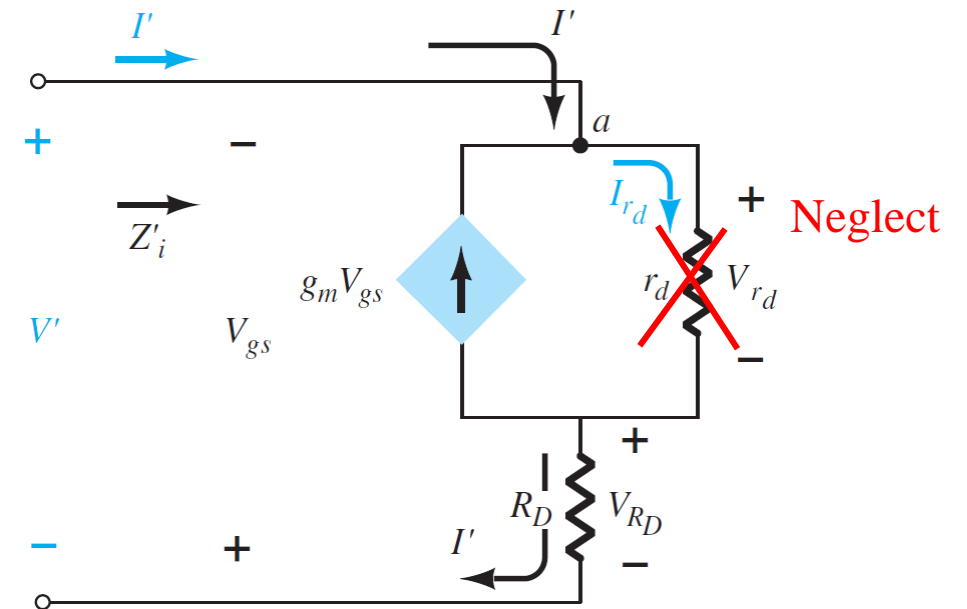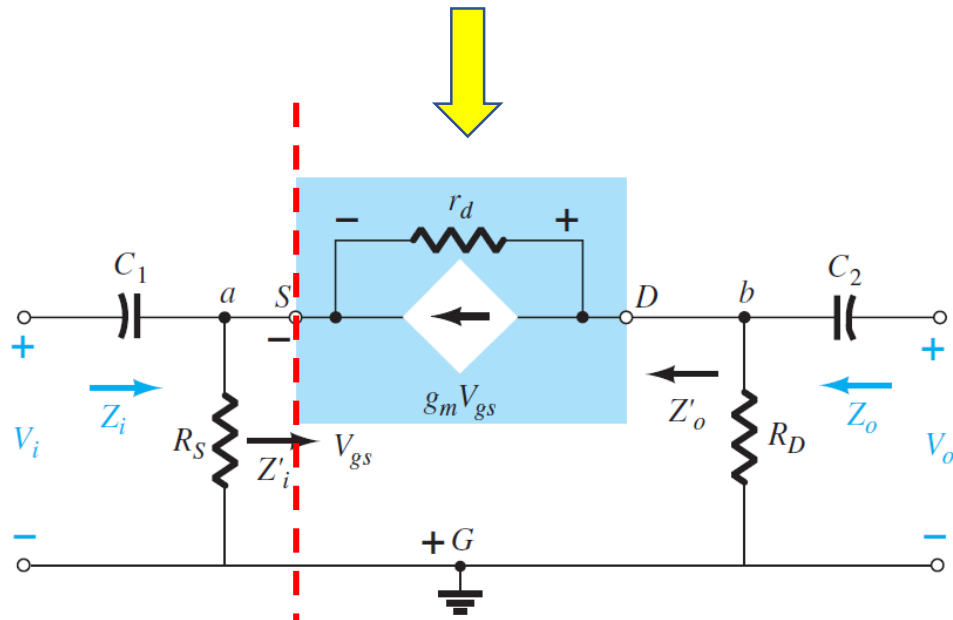
- The controlled source $g_m V_{gs}$ be connected from drain to source
- No isolation between input and output



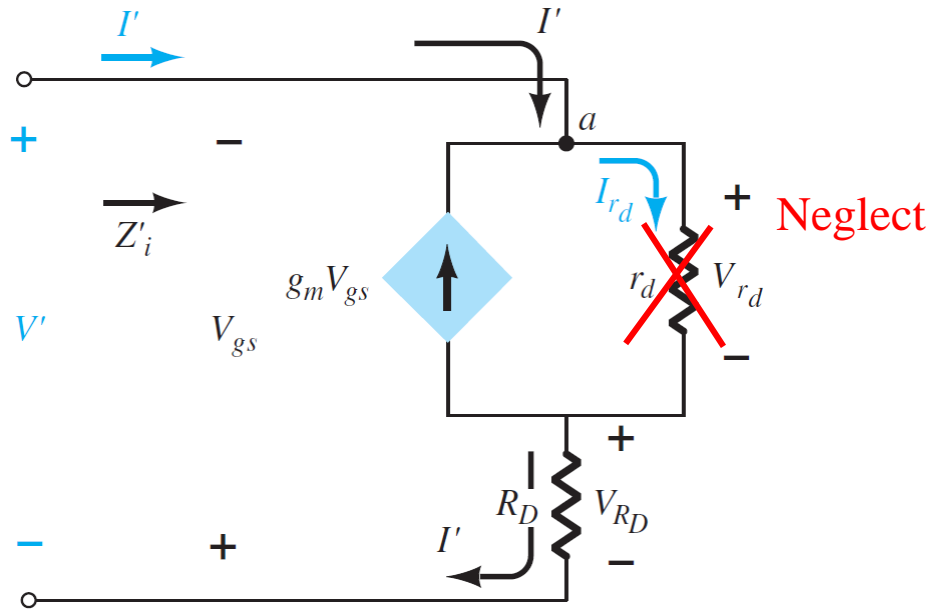


$$Z'_i = \frac{V'}{I'} = \frac{V_{RD}}{g_m V_{gs}} \quad ; V_{RD} = V_{gs}$$

$$= \frac{1}{g_m}$$

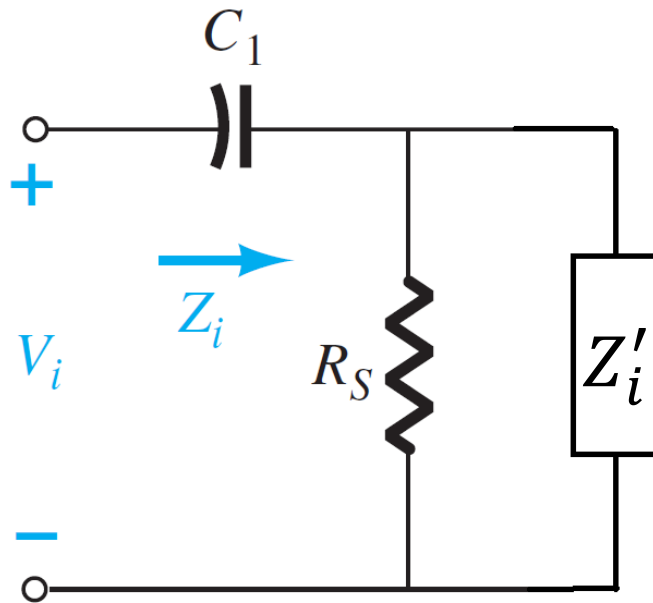

$$Z_i \cong R_S \parallel 1/g_m$$

Find Z_o , A_v

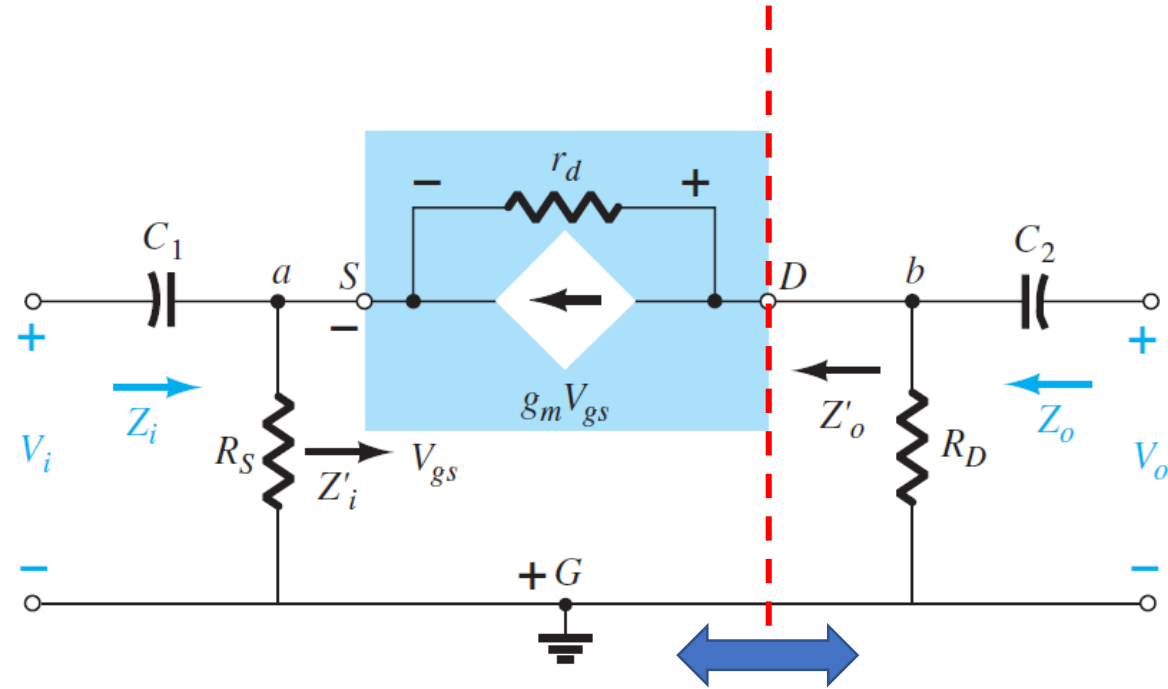

Give $V_i = 0 \implies V_{gs} = 0$

No current flow

$$Z_o = R_D$$

A_v : Consider Node b

$$I_D + g_m V_{gs} = 0$$

$$I_D = -g_m V_{gs}$$

$$= g_m V_i$$

$$V_o = I_D R_D$$

$$= g_m V_i R_D$$




$$\frac{V_o}{V_i} = g_m R_D$$

A_v





means in-phase

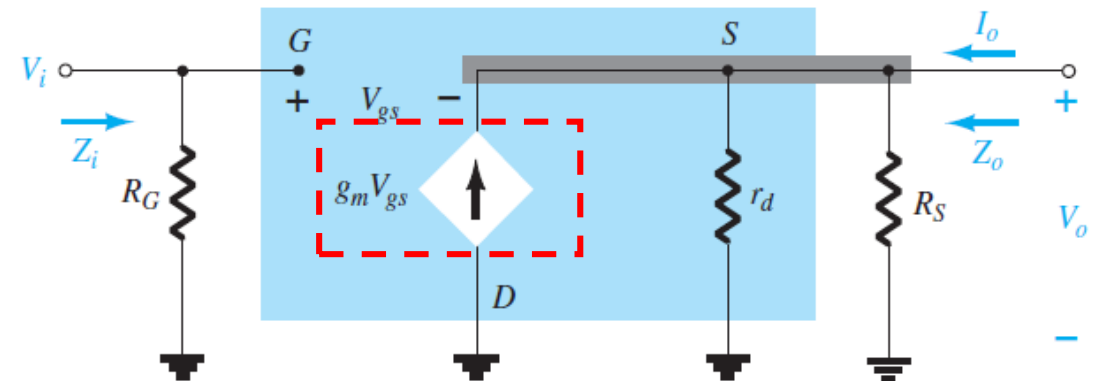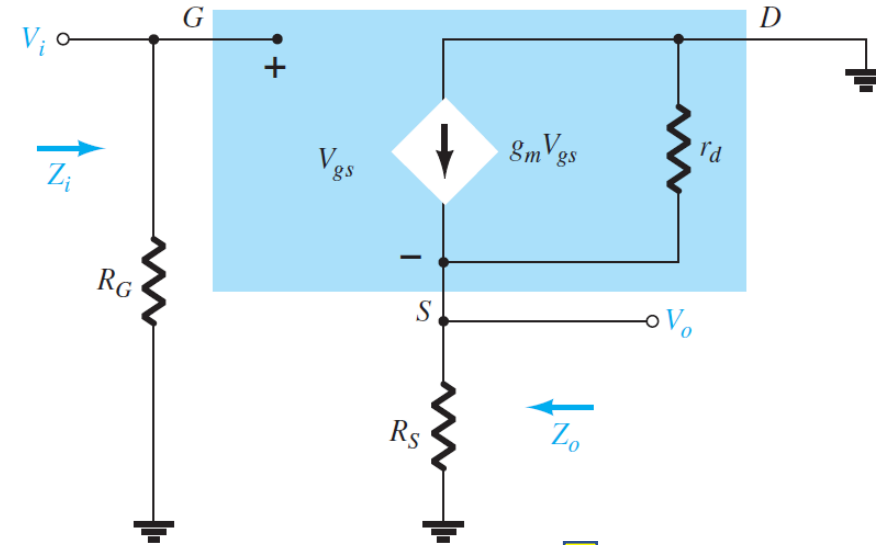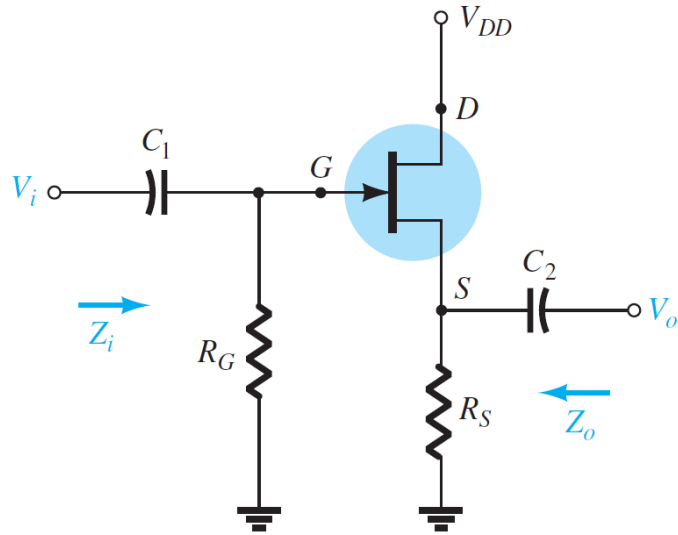SOURCE-FOLLOWER (COMMON-DRAIN) CONFIGURATION



- BJT emitter-follow configuration
- V_o out from source (normally from drain)
- Short V_{DD} to ground \rightarrow Drain to ground

Find Z_i , Z_o , A_v

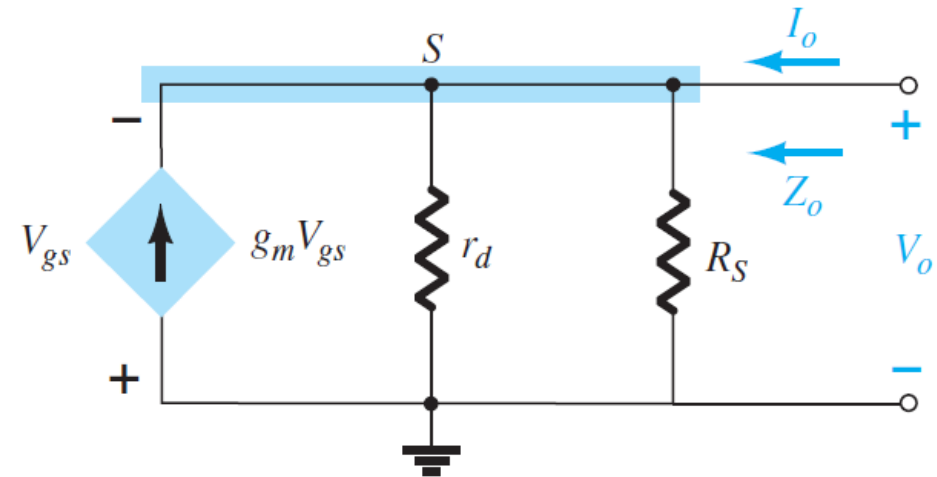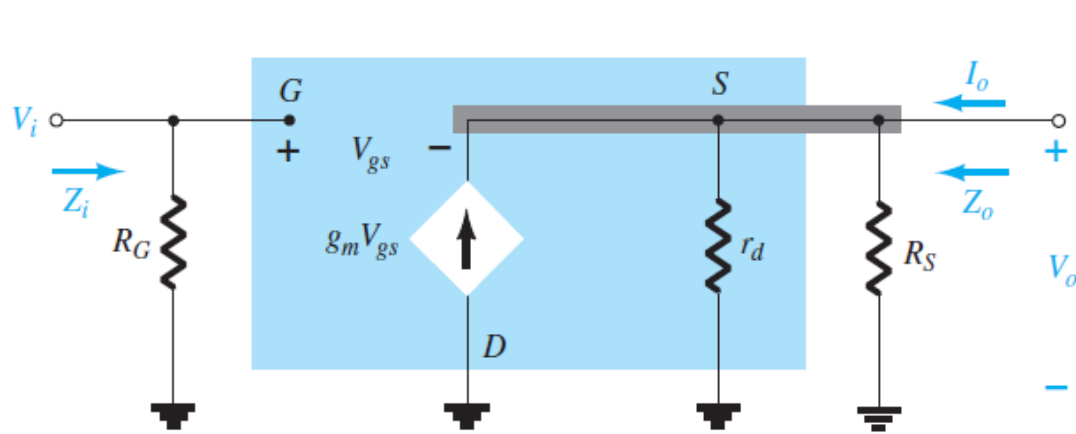


$$Z_i = R_G$$

$$Z_o = \frac{V_o}{I_o} = \frac{V_o}{V_o \left[\frac{1}{r_d} + \frac{1}{R_S} + g_m \right]} = \frac{1}{\frac{1}{r_d} + \frac{1}{R_S} + g_m} = \frac{1}{\frac{1}{r_d} + \frac{1}{R_S} + \frac{1}{1/g_m}}$$

$$V_o = -V_{gs}$$
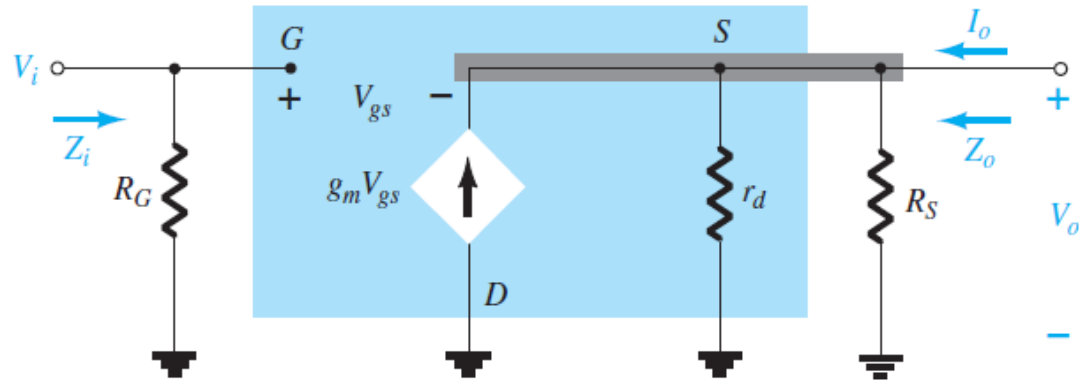
$$Z_o = r_d \parallel R_S \parallel 1/g_m$$



$$V_o = g_m V_{gs} (r_d \parallel R_S)$$

Consider outer loop

$$V_i = V_{gs} + V_o$$

$$V_{gs} = V_i - V_o$$

$$V_o = g_m (V_i - V_o) (r_d \parallel R_S)$$

$$= g_m V_i (r_d \parallel R_S) - g_m V_o (r_d \parallel R_S)$$

$$V_o [1 + g_m (r_d \parallel R_S)] = g_m V_i (r_d \parallel R_S)$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m (r_d \parallel R_S)}{1 + g_m (r_d \parallel R_S)}$$

Gain always < 1