

General Electronics II

3rd April 2018 (Tue.)

Room: E202 10:30-12:00






ผู้สอน : คร. อัจฉรา พิเชฐจำเริญ

BJT AC Analysis


Outline:

- Review of ac
- r_e model
- Common-Emitter Fixed-Bias Configuration
- Voltage-Divider Bias
- CE Emitter-Bias Configuration

AC waveform

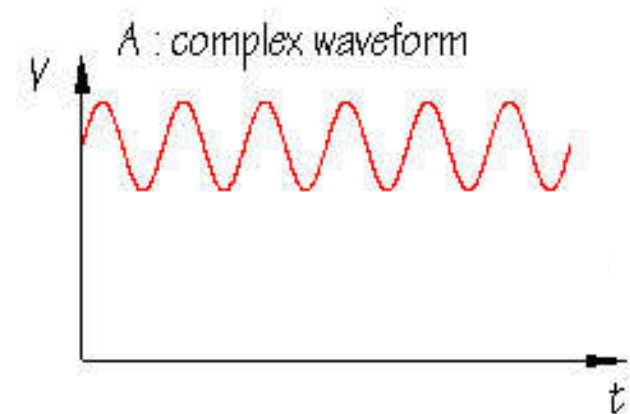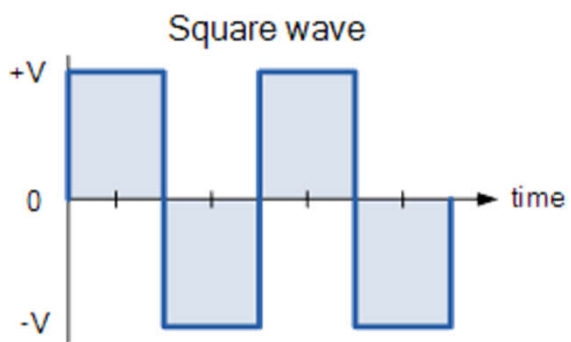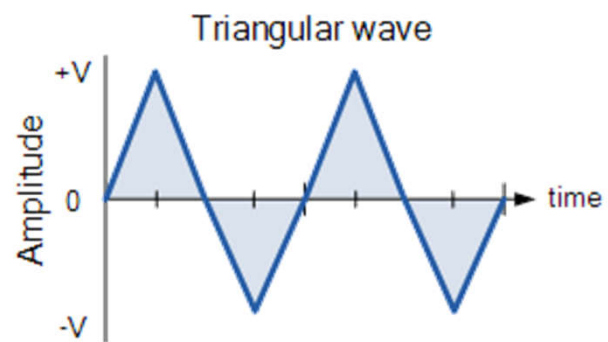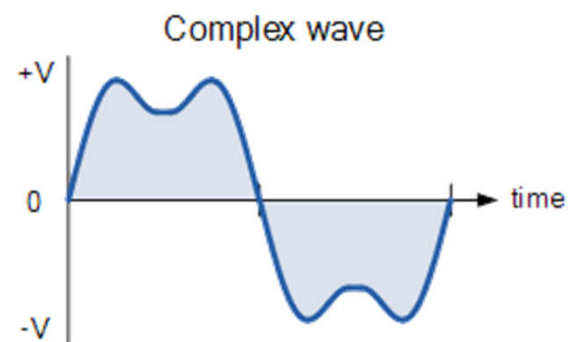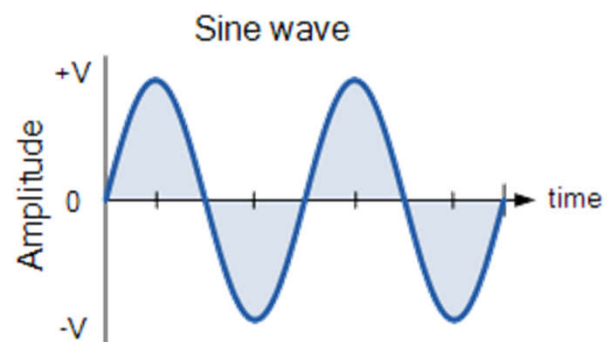


Review:

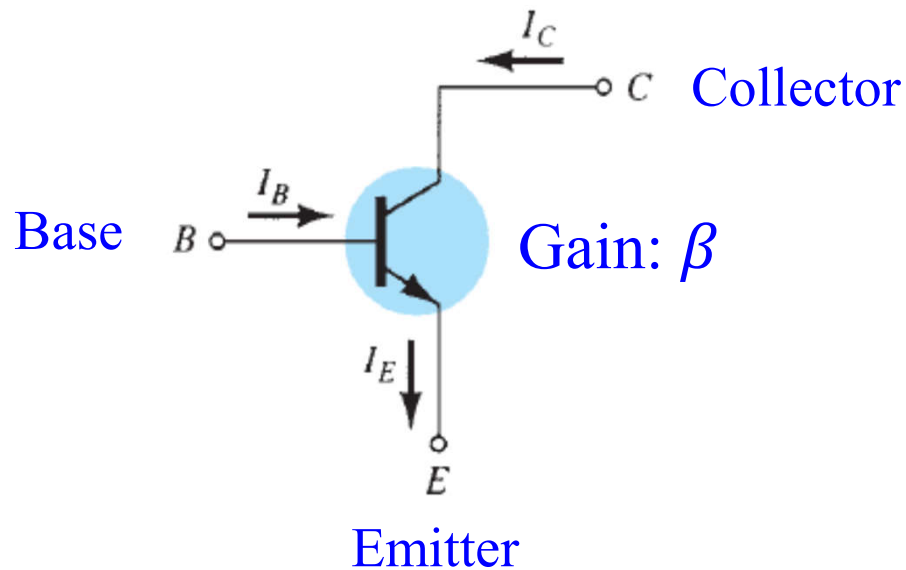

How large of I_C , I_B , I_E ?

BJT = Current control device

FET = Voltage control device

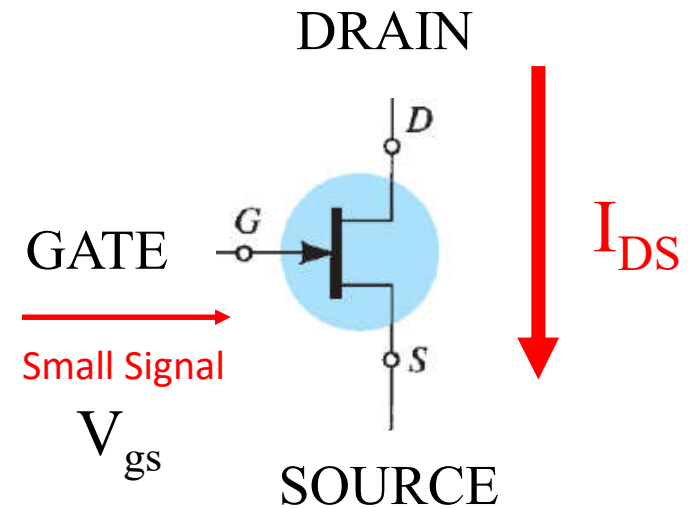

BJT has β (beta)


FET has g_m transconductance factor

Amplifier Modeling:


- Approximation of device behavior to Equivalent circuit.
 - Apply with circuit analysis theory to solve the parameters.
1. Hybrid Equivalent Network \rightarrow data sheet data
 2. r_e model \rightarrow actual operation data but no feedback terms
 3. Two-port system

r_e Transistor Model


Common-Emitter Fixed-Bias Configuration

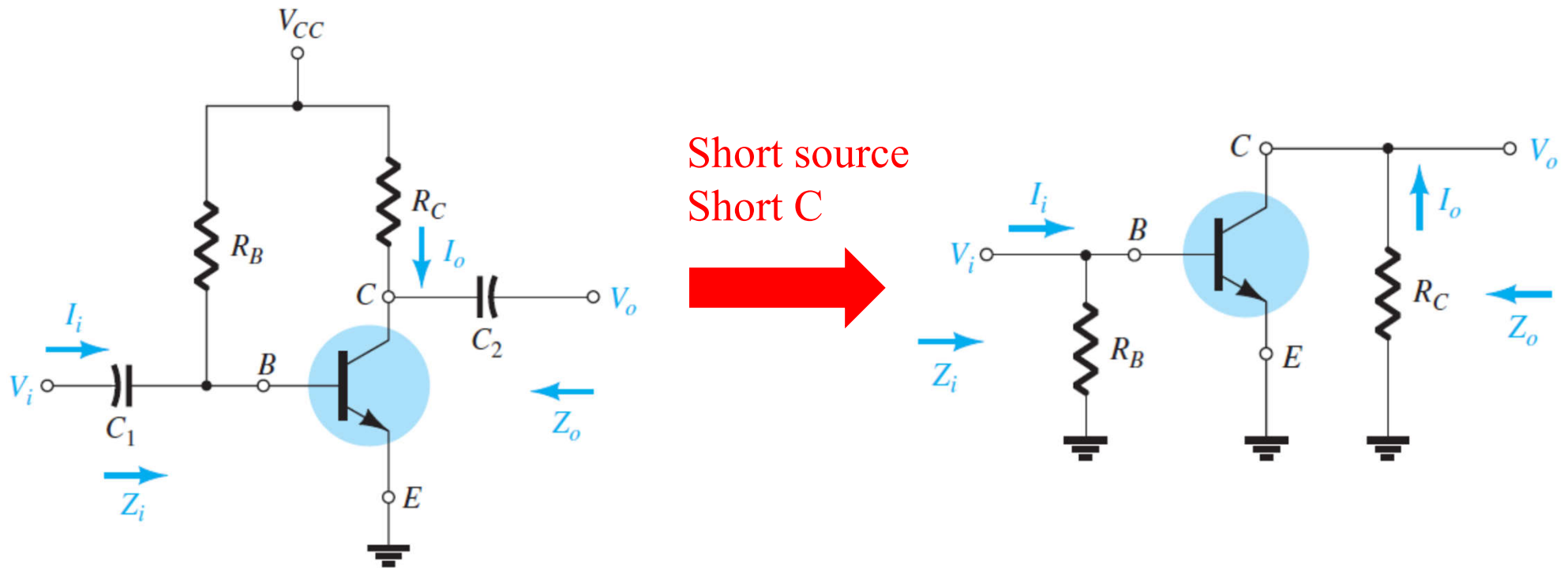

Transform to r_e model

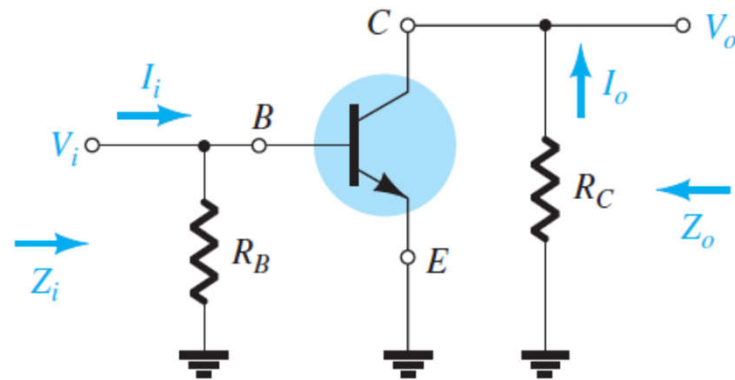

Parameters

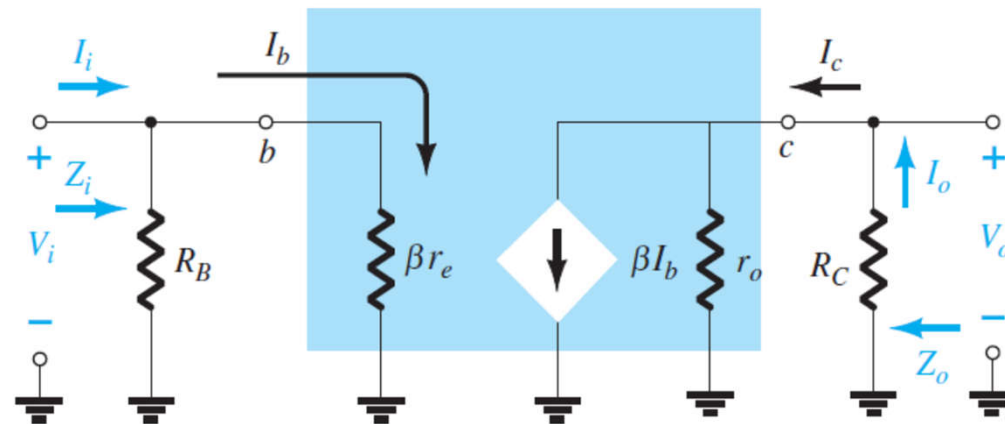


$$Z_i =$$


$$r_e = \frac{26 \text{ mV}}{I_E}$$

$$V_i = 0 ; \quad Z_o =$$

$$A_v =$$

180° phase shift

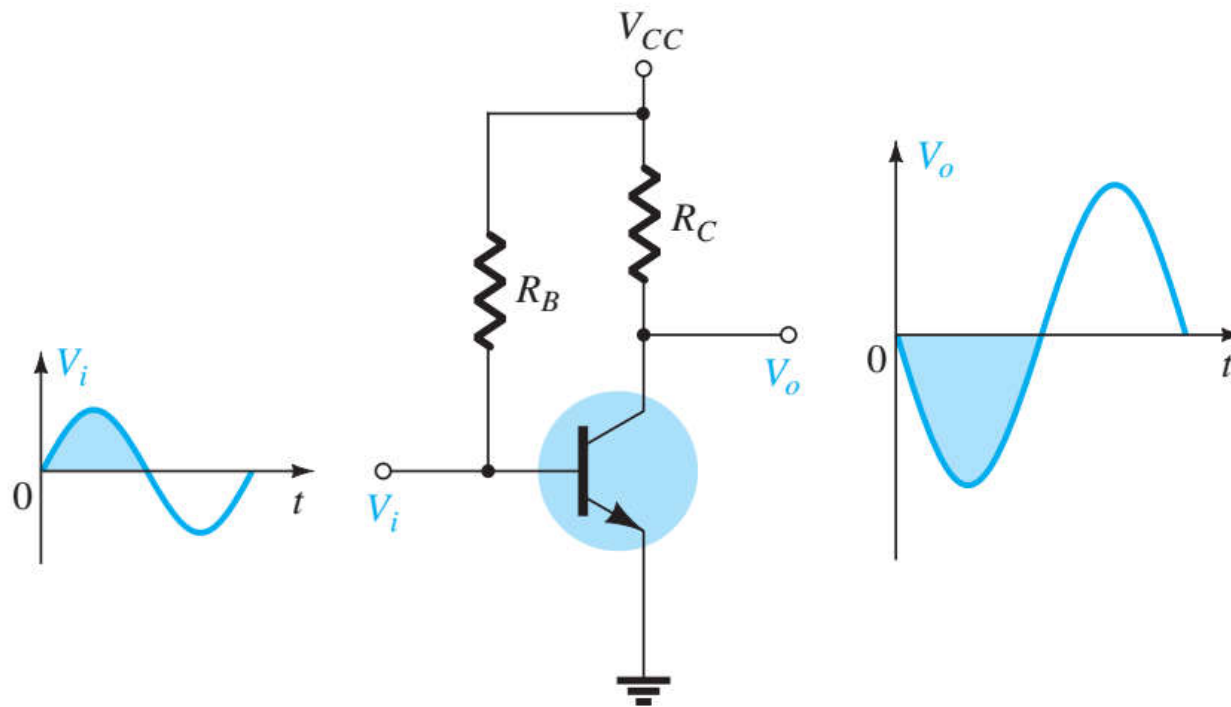

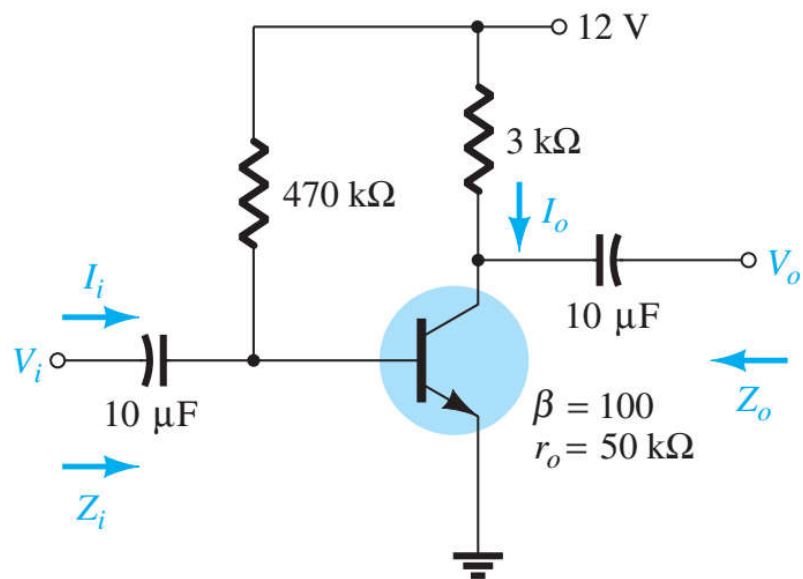

- Determine r_e .
- Find Z_i (with $r_o = \infty \Omega$).
- Calculate Z_o (with $r_o = \infty \Omega$).
- Determine A_v (with $r_o = \infty \Omega$).
- Repeat parts (c) and (d) including $r_o = 50 \text{ k}\Omega$ in all calculations and compare results.

VOLTAGE-DIVIDER BIAS

